

1. The following karnaugh map represent a function F .

		F			
		00	01	11	10
X	0	1	1	1	0
	1	0	0	1	0

Figure 1: function

Which of the following circuits is a realization of the above function F

